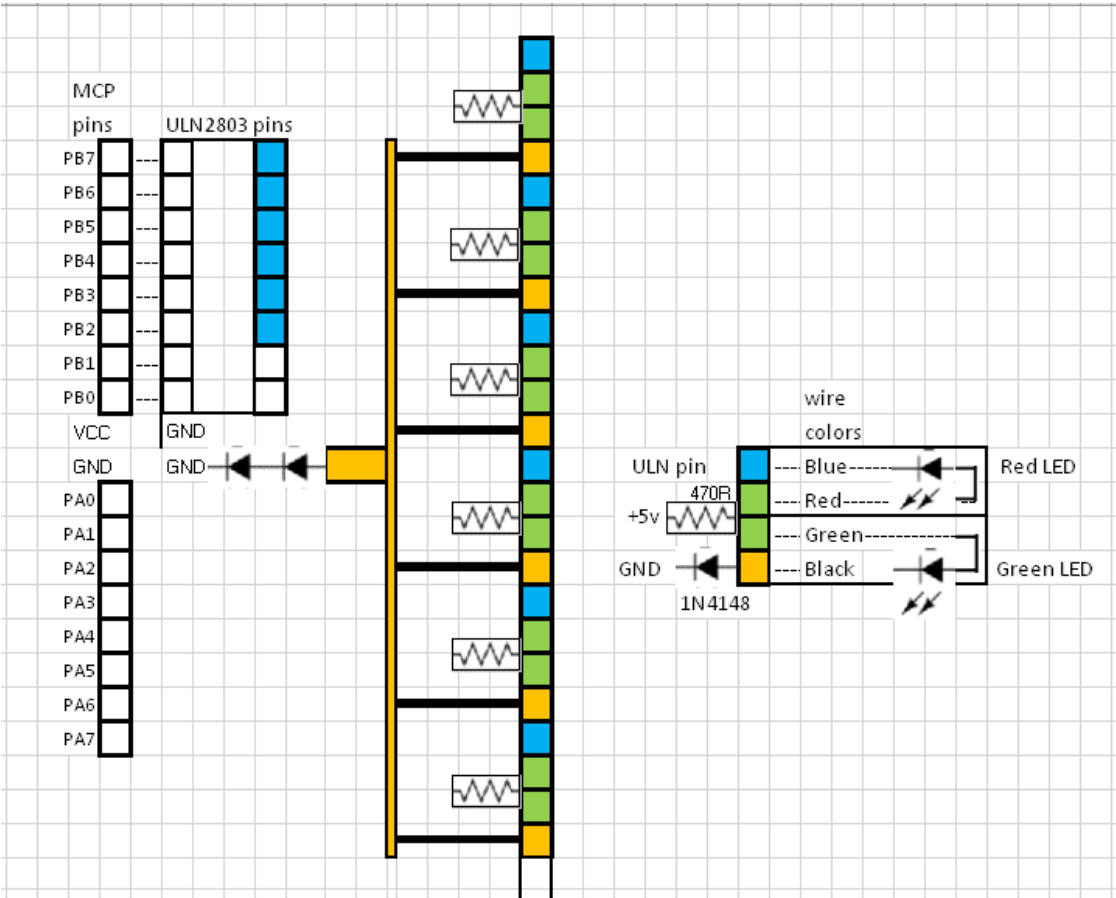


Mimic panel - one output switches two LEDs between RED/GREEN



Similar circuit using transistor instead of Darlington transistor array. Different resistor for 12V.
R3 and R4 resistors are internal in the IC, when using ULN2803.

